

BJT**Collector current**

$$I_C = \frac{A_E q D_n n_i^2}{N_E W_B} \left(\exp\left(\frac{V_{BE}}{V_T}\right) - 1 \right)$$

$$I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right)$$

Base emitter voltage

$$V_{BE} = V_T \ln \frac{I_C}{I_S}$$

Thermal Voltage

$$V_T = 26mV$$

Transconductance

$$g_m = \frac{I_C}{V_T}$$

Output Impedance (Early Effect)

$$R_O = \frac{V_A}{I_S \exp\left(\frac{V_{BE}}{V_T}\right)} \approx \frac{V_A}{I_C}$$

Internal Small Signal Resistance

$$r_\pi = \frac{\beta}{g_m} = \beta \frac{V_T}{I_C}$$

Terminal Currents

$$I_E = I_C + I_B$$

$$I_C = \beta I_B$$

Input Impedances

Into Base, Emitter AC Grounded

Into Collector, Emitter AC Grounded

 ∞

Into Collector, Emitter AC Grounded (Early)

 r_o

Into Emitter, Base AC Grounded

$$\frac{1}{g_m}$$

Degenerated CE Stage

$$r_\pi + (\beta + 1)R_E$$

Self Biased Stage

$$r_\pi \parallel \frac{1}{g_m}$$

Degenerated CE Stage (early)

$$R_{out} \approx r_o [1 + g_m (R_E \parallel r_\pi)]$$

Common Base

Core

$$A_V = g_m R_C$$

With Source Resistance

$$A_V = \frac{R_C}{\frac{1}{g_m} + R_S}$$

Output Impedance (Early)

$$R_{out1} = [1 + g_m (R_E \parallel r_\pi)] r_o + (R_E \parallel r_\pi)$$

$$R_{out} = R_C \parallel R_{out1}$$

Output Impedance of CB/CE are same if under same condition

Emitter Follower (Common Collector)

Output Resistance

$$R_{out} = \left(\frac{R_S}{\beta + 1} + \frac{1}{g_m} \right) \parallel R_E \parallel r_o$$

CMOS**Drain Current**

Saturation No Channel Length Modulation

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$$

Saturation With Channel Length Modulation

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$$

Triode Region

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} [2(V_{GS} - V_{TH})V_{DS} + V_{DS}^2]$$

Transconductance

$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})$$

$$g_m = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D}$$

$$g_m = \frac{2I_D}{V_{GS} - V_{TH}}$$

Gain

$$A_V = g_m R_D$$

Linear Resistance (Deep Triode Region)

$$R_{on} = \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})}$$

Channel Length Modulation

$$R_o = \frac{1}{\lambda I_{DS}}$$

Regions of Operation

N-Channel Cut Off

$$V_{GS} \leq V_T$$

N-Channel Linear

$$V_{GS} > V_T, V_{DS} \leq V_{GS} - V_T$$

N-Channel Saturation

$$V_{GS} > V_T, V_{DS} > V_{GS} - V_T$$

P-Channel Cut Off

$$V_{SG} \leq |V_T|$$

P-Channel Linear (Triode)

$$V_{SG} > |V_T|, V_{SD} \leq V_{SG} - |V_T|$$

P-Channel Saturation

$$V_{SG} > |V_T|, V_{SD} > V_{SG} - |V_T|$$

Common Source

$$A_V = \frac{-R_D}{\frac{1}{g_m} + R_S}$$

Current Mirrors

Output Impedance Bipolar

$$R_{out} = [1 + g_m(R_E||r_\pi)]R_o + R_E||r_\pi$$

Output Impedance Bipolar Cascode

$$\begin{aligned} R_{out} &= [1 + g_{m1}(r_{o2}||r_{\pi1})]r_{o1} + r_{o2}||r_{\pi1} \\ &\approx g_{m1}r_{o1}(r_{o2}||r_{\pi1}) \end{aligned}$$

Maximum limited by beta and r_o

$$R_{out,max} = \beta_1 r_{o1}$$

Improved Cascode using PNP current source

$$R_{out} \approx g_{m3}r_{o3}(r_{o4}||r_{\pi3})||g_{m2}r_{o2}(r_{o1}||r_{\pi2})$$

Output Impedance CMOS

$$R_{out} = R_S + (1 + g_m R_S) r_o$$

Output Impedance CMOS Cascode

$$\begin{aligned} R_{out} &= (g_{m1}r_{o2})r_{o1} + r_{o2} \\ &\approx g_{m1}r_{o1}r_{o2} \end{aligned}$$

Improved Cascode using PMOS current source

$$R_{out} \approx g_{m3}r_{o3}r_{o4}||g_{m2}r_{o2}r_{o1}$$

Short Circuit Transconductance

$$G_m = \frac{i_{out}}{V_{in}}$$

$$A_v = -G_m R_{out}$$

Cascode Amplifier CMOS

$$G_m = g_{m1}$$

Current Mirror

$$I_{copy} = \frac{nI_{REF}}{1 + \frac{1}{\beta}(n+1)}$$

With an extra transistor to reduce error

$$I_{copy} = \frac{nI_{REF}}{1 + \frac{1}{\beta^2}(n+1)}$$

Differential Amplifiers

Bipolar Differential Amplifier

LSA Current

$$\begin{aligned} I_{C1} &= \frac{I_{EE} \exp \frac{V_{in1} - V_{in2}}{V_T}}{1 + \exp \frac{V_{in1} - V_{in2}}{V_T}} \\ I_{C2} &= \frac{I_{EE}}{1 + \exp \frac{V_{in1} - V_{in2}}{V_T}} \end{aligned}$$

Linear Operation Mode

$$|V_{in1} - V_{in2}| < 4V_T \approx 104mV$$

Small Signal Mode

$$|V_{in1} - V_{in2}| < 10mV$$

MOS Differential Pair

Maximum Differential Input Voltage

$$|V_{in1} - V_{in2}|_{max} = \sqrt{2}(V_{GS} - V_{TH})_{equil}$$

Small Signal Mode

$$|V_{in1} - V_{in2}| \ll \frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}}$$

Common mode to Differential Mode

$$A_{CM-DM} = \frac{\Delta R_D}{\frac{1}{g_m + 2R_{SS}}} \approx \frac{\Delta R_D}{2R_{SS}}$$

Frequency Response

Miller's Theorem

$$Z_1 = \frac{Z_F}{1 - A_V}$$

$$Z_2 = \frac{Z_F}{1 - \frac{1}{A_V}}$$

$$C_{in} = (1 - A_v)C_F$$

$$C_{out} = (1 - \frac{1}{A_v})C_F$$

Transit Frequency


BJT

$$2\pi f_T = \frac{g_m}{C_{GS}}$$

CMOS

$$2\pi f_T = \frac{g_m}{C_\pi}$$

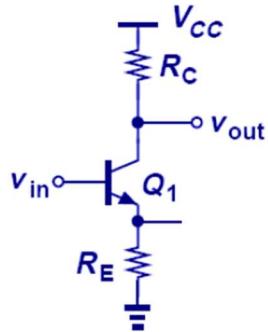RECAP: Degenerated CE Stage with Resistive divider




Without series resistance

$$A_v = -\frac{R_c}{\frac{1}{g_m} + R_E}.$$

$$R_{in} = r_\pi + (\beta + 1)R_E$$

$$R_{out} = R_C$$

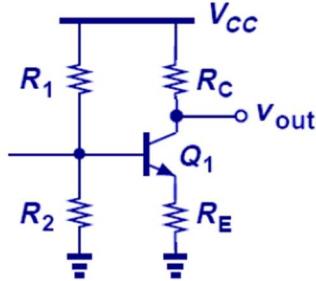


With resistive divider

$$A_v = -\frac{R_c}{\frac{1}{g_m} + R_E}.$$

$$R_{in} = [r_\pi + (\beta + 1)R_E] \parallel R_1 \parallel R_2,$$

$$R_{out} = R_C$$

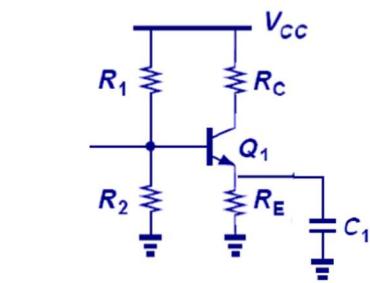

With resistive divider & C1


$$A_v = -g_m R_C$$

$$R_{in} = r_\pi \parallel R_1 \parallel R_2$$


$$R_{out} = R_C.$$

AMPLIFIER TYPE	COMMON BASE	COMMON Emitter	COMMON Emitter (Emitter Resistor)	COMMON COLLECTOR (Emitter Follower)
INPUT/OUTPUT PHASE RELATIONSHIP	0°	180°	180°	0°
VOLTAGE GAIN	HIGH $\frac{\alpha R_c}{R_s + r_e}$	MEDIUM $\frac{\beta (R_c \parallel r_o)}{R_s + r_e}$	MEDIUM $\frac{\beta R_c}{R_s + (\beta + 1)(r_e + R_E)}$	LOW $\frac{(\beta + 1)(R_L \parallel r_o)}{R_s + (\beta + 1)[r_e + (R_L \parallel r_o)]}$
CURRENT GAIN	LOW α	MEDIUM $\beta \frac{r_o}{R_c + r_o}$	MEDIUM β	HIGH $(\beta + 1) \frac{r_o}{r_o + R_L}$
POWER GAIN	LOW	HIGH	HIGH	MEDIUM
INPUT RESISTANCE	LOW r_e	MEDIUM $r_e = (\beta + 1)r_e$	MEDIUM $(\beta + 1)(r_e + R_E)$	HIGH $(\beta + 1)[r_e + (r_e \parallel R_L)]$
OUTPUT RESISTANCE	HIGH R_c	MEDIUM $R_c \parallel r_o$	MEDIUM R_c	LOW $r_o \parallel \left[r_e + \frac{R_s}{(\beta + 1)} \right]$


Voltage Gain Equations

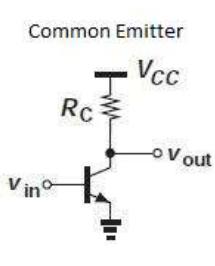


$$A_v = -g_m (R_C \parallel r_O)$$

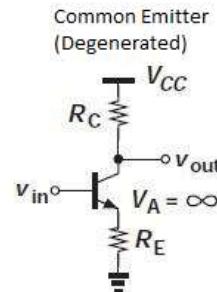

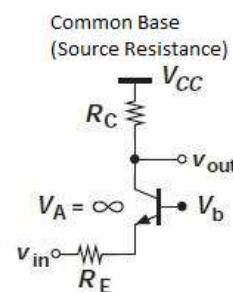
$$A_v = -\frac{R_C}{\frac{1}{g_m} + R_E}$$



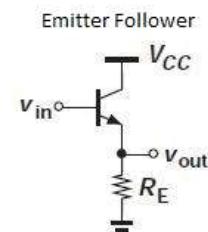
$$A_v = \frac{R_C}{\frac{1}{g_m} + R_E}$$



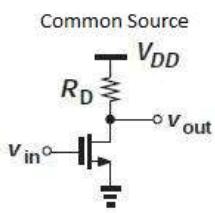
$$A_v = \frac{R_E \parallel r_O}{\frac{1}{g_m} + R_E \parallel r_O}$$




$$A_v = -g_m (R_D \parallel r_O)$$

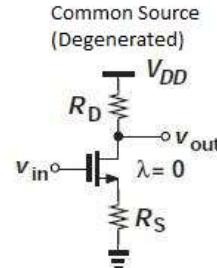
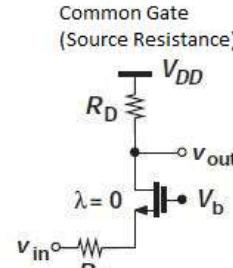
$$A_v = -\frac{R_D}{\frac{1}{g_m} + R_S}$$


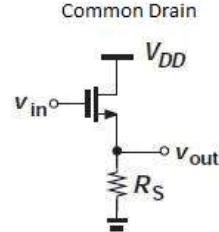
$$A_v = \frac{R_D}{\frac{1}{g_m} + R_S}$$



$$A_v = \frac{R_S \parallel r_O}{\frac{1}{g_m} + R_S \parallel r_O}$$